



UNIVERSITÀ DEGLI STUDI DI TRENTO

GROUP MAR01

REPORT OF THE EXPERIMENTS PERFORMED IN THE COURSE OF PHYSICS LABORATORY III

Authors:

Canteri Marco

Biasi Lorenzo

Luca Vespucci

Professor:

Rolly Grisenti

October 26, 2016

Contents

1	Basic circuits with an operational amplifier	2
1.1	Materials	2
1.2	Experiment setup	2
1.3	Data analysis	4
2	Let's get more confident with our little friend op-amp	7
2.1	Materials	7
2.2	Experiment setup	7
2.3	Data analysis	10
3	Unfortunately the op-amp is not so ideal	13
3.1	Materials	13
3.2	Experiment setup	13
3.3	Data analysis	15
4	Gain in function of the frequency	18
4.1	Materials	18
4.2	Experimental setup	18
4.3	Data Analysis	19
5	Introducing the comparator	21
5.1	Materials	21
5.2	Experimental setup	21
5.3	Data Analysis	23
6	Resistance thermometer	25
6.1	Materials	25
6.2	Experimental setup	25

Experiment 1

Basic circuits with an operational amplifier

In this experiment we have built five different circuits. The first is an open loop circuit with the operational amplifier uA741, the goal was to find the maximum voltage output by the op-amp. The last four circuits are in closed loop configuration with a negative feedback, they consist in a follower, a non inverting amplifier, an inverting amplifier and a weighted summing amplifier. We have measured the voltage input and the voltage output of every circuit.

1.1 Materials

- Operational amplifier uA741
- Resistors, nominal value: $100\ \Omega$, $220\ \Omega$
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Oscilloscope AGILENT 54261A

1.2 Experiment setup

In the first four circuits the output of the waveform generator was a sine wave of 100Hz frequency and a peak-peak voltage of 100mV. We measured the waveform input signal v_{in} and the output voltage v_o of the op-amp. The measurements were performed using an oscilloscope triggered externally, the signal acquired is an 8 cycles average. The voltage supply of the op-amp was set to $v_{cc} = 15\text{V}$ for all the circuits.

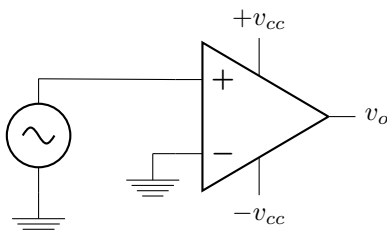


Figure 1.1: Open loop circuit

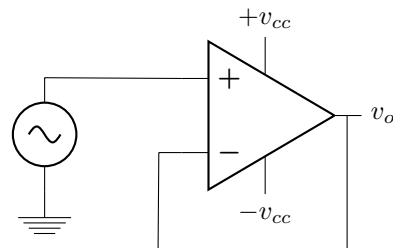


Figure 1.2: Follower

 


Figure 1.3: Non inverting amplifier

 


Figure 1.4: Inverting amplifier

For the last circuit we used another sine wave signal with the same 100Hz frequency and a different peak-peak voltage. The oscilloscope's setting and the measurement taken was the same as before. The values of the resistor are: $R_1 = 99.89 \pm 0.02 \Omega$, $R_2 = 218.37 \pm 0.04 \Omega$, $R_3 = 99.89 \pm 0.02 \Omega$ (the measurement were made with the multimeter).

 


Figure 1.5: Weighted summing amplifier

1.3 Data analysis

 


Figure 1.6: Open loop configuration

In the open loop configuration we get an output (visible in the figure one) that has a max absolute value of 14.35 ± 0.16^1 V and a minimum value of -12.94 ± 0.16^1 V. In the ideal model we would expect the output to be infinite, as justified from the equation $v_o = A_{ol}(v_+ - v_-)$ where A_{ol} tends to infinity. In the physical case the output voltage is constrained by the saturation voltage that's determined by the voltage applied to the op-amp. The minimum and maximum value of the output have different absolute value, due to the lack of symmetry between the *nnp* and *pnp* transistors in the final push-pull stage of the op-amp.

 


Figure 1.7: Emitter follower

¹Error based on oscilloscope's 8 bit resolution

In the emitter follower we expect, ideally, an output voltage equal to the input one. But we can see in the plot a small discrepancy between the two signals: that is determined probably by the op-amp's offset, as we can see a downward translation in the output, and also by some other non ideal features of the op-amp.

 


Figure 1.8: Non-inverting amplifier

In the non-inverting amplifier configuration we expect the output to be: $v_o = v_{in}(1 + \frac{R_2}{R_1})$. The theoretical value calculated using the v_{in} and R_2, R_1 is 320.3 ± 1.9 mV. This prediction is not compatible with the output measured 313.4 ± 0.8 mV, probably because the op-amp is not ideal.

 


Figure 1.9: Inverting amplifier

In the inverting amplifier the output should be : $v_o = -v_{in} \frac{R_2}{R_1}$. The pk-pk of the output is 219.4 ± 0.8 mV that is compatible with theoretical value 219.8 ± 1.9 mV.

 


Figure 1.10: Weighted summing circuit

In the circuit (1.5) we used two inputs for acquiring an output voltage. This configuration sums these signals $v_1 = 135.1 \pm 0.8$ mV and $v_2 = 101.3 \pm 0.8$ mV using the resistors R_1 and R_3 as weights, giving as output $v_o = -R_2(\frac{v_1}{R_1} + \frac{v_2}{R_3})$, which gives a pk-pk value of 516.7 ± 2.7 mV. The theory in this case it's not at all compatible with the measurement 506 ± 0.8 mV, but that's, most likely, caused by the noise in the output.

Experiment 2

Let's get more confident with our little friend op-amp

We designed a non-inverting amplifier with a variable gain by using a trimmer. The second circuit designed was a summing amplifier with an unitary gain. We built a current source generator of 1 mA and tested it with a variable load. We tested the efficacy of the emitter follower configuration in mismatching the source's impedance. Last we designed a differential amplifier with a predetermined gain.

2.1 Materials

- Operational amplifier uA741
- Resistors and trimmers
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Oscilloscope RIGOL MS02102A
- Two capacitance of nominal value of 100nF

2.2 Experiment setup

In each circuit we powered the op-amp with a ± 15 V DC voltage and, in order to reduce possible noises, we added two 100nF capacitors connecting the op-amp's pins for the power supply with the ground. The input signal has a frequency of 100 Hz and a peak-peak voltage of 1V except for the differential amplifier. For every specific circuit we designed them as follow:

- Inverting amplifier: we placed a $10\text{k}\Omega$ trimmer along the feedback branch in series to a resistor $R_f = 983.9 \pm 0.1\Omega$. In order to have a minimal gain of 5, we used $R_{in} = 199.84 \pm 0.03\Omega$ as in figure (2.1).
- Summing amplifier: caring for the simplest calculations, we used $R_1 = 1484.7 \pm 0.2\Omega \simeq R_2 = 1483.5 \pm 0.2\Omega$ so the equation is $\frac{v_1 + v_2}{2} \left(1 + \frac{R_4}{R_3}\right)$. For obtaining the sum of the input in output, we had to choose $R_3 = R_4 = 1001.3 \pm 0.1\Omega$. The inputs v_1 and v_2 are the same 100 Hz, 1 V peak-peak sine wave signal.

 


Figure 2.1: Inverting variable amplifier

 


Figure 2.2: Non-inverting summing amplifier, unitary gain

- Emitter follower test: at first we built a circuit without the emitter follower using an input impedance of $R = 100.2 \pm 1 \text{ k}\Omega$ and a load of $R_L = 19.8 \pm 2 \text{ k}\Omega$. Then we added the op-amp stage and compared the output measurements in the 2 different cases.

 


Figure 2.3: Test circuit without follower

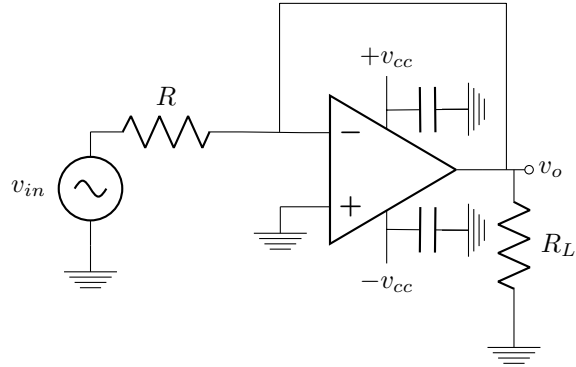


Figure 2.4: Test circuit with follower

- Current generator: the aim of this circuit is to generate a stable fixed current independent from the load. We generated a 1 mA current using a DC voltage source of 5 V and a $4.9693 \pm 0.7 \text{ k}\Omega$ resistor. The load was simulated with a trimmer.
- Differential amplifier: the full equation the circuit in figure (2.6) is the following:

$$v_o = \frac{R_F}{R_1} \left[\frac{v_b}{1 + R_f/R_y} \left(1 + \frac{R_1}{R_f} \right) - v_a \right]$$

we first set to ground v_b , in this way we were able to set up the gain of the circuit (we chose it to be $A = 2$ with $R_F = 3 \pm 0.2 \text{ k}\Omega$ (5% error of nominal value)). After that we put the same signal of v_a in v_b with a resistor R_f and a variable resistor R_y made with R_2 in series with a trimmer. We managed with the trimmer to get the output as close to zero as possible (Figure (2.7)). This means in the equation $R_f/R_y = R_1/R_F$ so the new output is exactly what we want $v_o = A(v_b - v_a)$. For testing the amplifier we used $v_a = 5 \text{ V}$ DC and for v_b a sine wave 1 V peak-peak 100 Hz with an offset of 5 V.

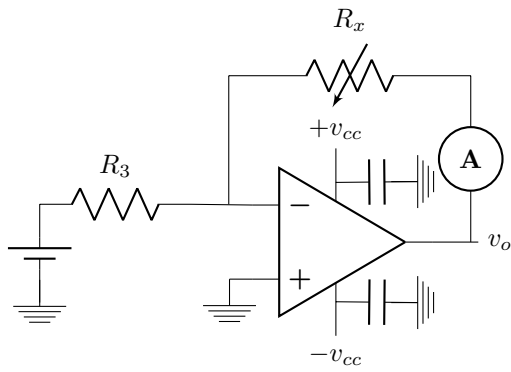


Figure 2.5: Current source generator

 


Figure 2.6: differential amplifier

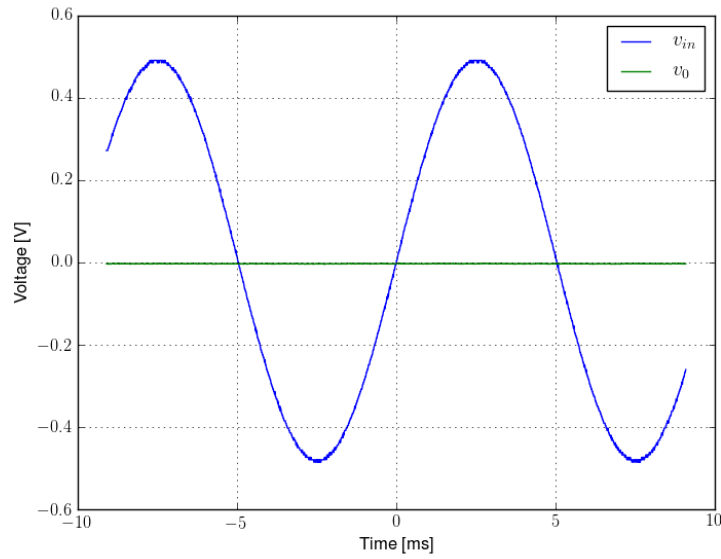


Figure 2.7: Calibration of the differential amplifier

2.3 Data analysis

 


Figure 2.8: Variable amplifier

In the inverting amplifier we used a trimmer in order to vary the gain, in fact the equation is:

$$v_o = -v_{in} \frac{R_f + R_x}{R_{in}}$$

so increasing R_x cause output to linear increasing. The output voltage is limited by the op-amps's power supply voltage, it cannot increase further and the signal goes flat, as we can see in figure (2.8) (light blue line), this behavior is called “Clipping”. The graphic also shows a discrepancy between the absolute value of maximum and minimum voltage during the clipping: this is due to the asymmetry between *pnp* and *nnp* transistors in the op-amp's final stage.

 


Figure 2.9: Weighted summing amplifier

EXPERIMENT 2. LET'S GET MORE CONFIDENT WITH OUR LITTLE FRIEND OP-AMP

In the non-inverting summing amplifier circuit we wanted the output to be the simple sum of the signals in entrance, that were identical: it means that the output signal must have double amplitude compared to the input one. The peak-peak voltage's theoretical expectation is 2.0496 ± 0.0009 V while the measured one is 2.032 ± 0.001 V. The incompatibility probably is due to the op-amp's non-ideality.

 


Figure 2.10: Emitter follower comparison

Let's now analyse the differences between circuits with and without follower stage. We can see in figure (2.10) that using the follower we obtain a replicated signal while without it the signal is shrunk due to the input impedance, in fact the op-amp stage's purpose is the impedance mismatching.

In the current generator circuit we firstly measured the output current that was the expected one, than we observed the independency from the trimmer resistance of the current value.

 


Figure 2.11: Differential amplifier

EXPERIMENT 2. LET'S GET MORE CONFIDENT WITH OUR LITTLE FRIEND OP-AMP

In the differential amplifier circuit we measured an output cleared from the DC part present in the input, the output value was the AC part doubled compared to the input one. This is exactly how we expected the circuit to behave.

Experiment 3

Unfortunately the op-amp is not so ideal

In this set of experiments we dealt with the problems of a real op-amp such as the offset v_{os} , the bias currents i_{b+}, i_{b-} , the slew-rate, the maximum current output and the common gain A_{cm} , we performed the measures of these real parameters. The offset is studied with 3 different circuit and then compensated with a trimmer in the configuration suggested by the op-amp's datasheet. The bias currents was measured in two way, one for the bias current in the + 's op-amp input and one for the - 's op-amp input. The other parameters are studied simply adjusting the input for the measurement's purpose.

3.1 Materials

- Operational amplifier uA741
- Resistors, trimmer
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Oscilloscope RIGOL MS02102A

List of resistors used		
Resistor name	Value [Ω]	Uncertainty [Ω]
$R_{M\Omega}$	982.0×10^3	0.1×10^3
$R_{100k\Omega}$	99.22×10^3	0.01×10^3
$R_{10k\Omega}$	9906.2	1.2
$R_{k\Omega}$	1001.4	0.1
$R_{10\Omega}$	9.963	0.01
$R_{10k\Omega}^*$	9926.4	1.2
$R_{10\Omega}^*$	10.00	0.01

3.2 Experiment setup

In all the circuits we placed on the power supply's pins two capacitor each, one with high capacitace (nominal value 470 ± 23 nF) and one with low capacitance (10.0 ± 0.5 nF). These were used for suppressing the high-frequency noise and contrastig the effect of any eventual change in the voltage of the power supply, that could move the offset voltage.

 


Figure 3.1: Offset voltage's direct measure

 


Figure 3.2: Offset voltage's direct measure with gain

Figure 3.3: Offset voltage's direct measure with gain and bias current correction

In the first circuit we acquired v_{os} directly by measuring with the multimeter the output voltage. We used the second circuit to amplify v_{os} , thus we used the output to calculate v_{os} . The third circuit is identical to the second circuit except for the added resistors in parallel that connect + to the ground. This was done for removing the influence of the bias current in the measurement. Exploiting this last circuit we removed v_{os} by using a trimmer and trying to make the output closest that we could to 0.

 


Figure 3.4: Positive bias current measure

 


Figure 3.5: Negative bias current measure

The fourth circuit and fifth are used for measuring the current of bias indirectly using how the two currents are related to the output.

The sixth circuit was used for measuring the maximum current that the op-amp can erogate. In this configuration the oscilloscope's internal resitor was set to 50Ω

 


Figure 3.6: Max current measure

 


Figure 3.7: Slew rate

In the seventh circuit we measured the slew rate. As load the capacitor used was 1 ± 0.05 nF and the resistor 2 ± 0.1 k Ω . The input used was a 10 V square wave, so we acquired the image of the raising output.

In the last circuit we measured the common gain by using the differential amplifier with the same input 2 V peak-peak and 100 Hz.

 


Figure 3.8: Common Gain

3.3 Data analysis

In the emitter follower (3.1) the output measured is -1.484 ± 0.005 mV. Being such a small output we expect to have problem with parasite resistor and other form of noise, that's why we don't consider the output too reliable, but it gives us an order of magnitude that is in agreement with the datasheet of the op-amp, that propouses a typical value of 1 mV and a maximum value of 5 mV.

In the amplifier (3.2) we can find v_{os} , by using

$$v_{os} = \frac{v_o}{1 + \frac{R_{10k\Omega}}{R_{10\Omega}}}$$

from the calculation we get $v_{os} = -1.333 \pm 0.001$ mV, which is has the same order of magnitude and same sign of the previous result.

Then as stated in the experimental setup we corrected the circuit (3.3) for compensating the effect of the current of bias. With the same formula used for the previous amplifier we get an offset voltage of 1.307 ± 0.001 mV. We used this circuit for nulling the offset with the trimmer.

In the fourth circuit (3.4) we calculated the current flowing in the non invertent pin by using

$$i_{b+} = \frac{v_o}{R_{M\Omega}(1 + \frac{R_{100k\Omega}}{R_{1k\Omega}})}$$

EXPERIMENT 3. UNFORTUNATELY THE OP-AMP IS NOT SO IDEAL

The value calculated is -39.042 ± 0.009 nA.

In the fifth circuit (3.5) instead we calculate the current flowing in the invertent pin by using

$$i_{b-} = \frac{v_o}{R_{100k\Omega}} \frac{R_{k\Omega}}{R_{M\Omega}}$$

above the value is -39.724 ± 0.009 nA. Now we can compute the current of bias $i_b = \frac{|i_{b-}| + |i_{b+}|}{2} = 39.383 \pm 0.006$ nA and the offset current $i_o = ||i_{b-}| - |i_{b+}|| = 0.68 \pm 0.01$ nA. i_b is less than 100 nA and near the typical value of 10 nA, as the datasheet states, but the offset current is a bit low being around a third of the typical value 2 nA.

 


Figure 3.9: Saturated output caused by the maximum current erogated

In the sixth circuit (3.6) we calculated the maximum current erogated by computing the maximum/minimum output voltage over the resistance in the oscilloscope. In the plot is visible the different absolute value of the maximum and minimum output voltage, that's probably because the op-amp isn't perfectly symmetric in the packaging. So we opted to calculating two different maximum currents: $i_{max} = 0.0201 \pm 0.0001$ A (when the output was positive) and $i_{min} = 0.0328 \pm 0.0001$ (when the output was negative).

 


Figure 3.10: Saturated output caused by the maximum current erogated, red lines is 10% and 90% of the output

EXPERIMENT 3. UNFORTUNATELY THE OP-AMP IS NOT SO IDEAL

In the seventh circuit (3.7) we find that the slew rate of the op-amp used is $0.85 \frac{\text{V}}{\mu\text{s}}$, which is bigger than the typical value $0.5 \frac{\text{V}}{\mu\text{s}}$. One possible explanation of this would be that the slew rate depends on the amplitude of the signal, in our experiment the voltage was 50 times as large as in the test of visible in the datasheet, otherwise we have to conclude that our op-amp, has some difects that cause a larger slewrate.

 


Figure 3.11: Saturated output caused by the maximum current erogated

In the last circuit (3.8) we measured the commond gain, by using

$$A_{CM} = \frac{2v_o}{v_{in1} + v_{in2}}$$

which gave us an unitary gain, as it is evident in the plot.

Experiment 4

Gain in function of the frequency

In a real op-amp the open loop gain (A_{ol}) is a function of the input frequency. In this experience we explored systematically this behaviour using 2 different circuits, one for the lower frequencies and the other for the higher one. After this study we built a non inverting amplifier with ≈ 10 and ≈ 100 gain for measuring its bandwidth.

4.1 Materials

- Operational amplifier uA741
- Resistors, trimmer
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Oscilloscope RIGOL MS02102A

The resistor chosen were $R_1, R_2, R_3 = 10\text{k}\Omega$, $R_4 = 10\Omega$, $R_5 = 100\Omega$, $R_6 = 1\text{k}\Omega$ with an error of 5% of the value.

4.2 Experimental setup

 


Figure 4.1: A_{ol} measure low frequencies

 


Figure 4.2: A_{ol} measure high frequencies

In this experience we took the measurement in all circuits by changing the frequency of the input, that was a sine wave signal 1 V peak-peak. The voltage chosen is not important, because we are interested

in the ratio between the amplitude of two signal. In the first circuit was used for calculating the gain in the open loop configuration A_{ol} in low frequencies by measuring v_a and v_o . This circuit was chosen for low frequencies instead of the second one, because the gain is too high for allowing us to acquiring directly the voltage difference between the two input pins. We didn't measure at lower frequencies than 30 Hz because the noise didn't allow us to make a reliable estimate of the amplitude of the two signals.

In the second circuit we measured v_o and the voltage of the non inverting pin v_a . The frequencies measured went from 10 - 200 kHz, because with high frequencies the absolute value of A_{ol} is low enough.

In the last two circuits we built an non inverting amplifier with gain of 100 and 10.


 


Figure 4.3: Non inverting amplifier

4.3 Data Analysis

 

In the first circuit we can estimate the open loop gain by using $A_{ol} = -\frac{v_o}{v_a} \frac{R_3+R_4}{R_4}$. In the second circuit we calculated $A_{ol} = -\frac{v_o}{v_a}$.

We can see from the plot that the data appears to be on a straight line, we can also see if that line is compatible with the values in the datasheet. We can compute the theoretical open loop gain with:

$$A_{ol}^{teo}(f) = \frac{A}{1 + j \frac{f}{f_0}}$$

EXPERIMENT 4. GAIN IN FUNCTION OF THE FREQUENCY

Where $f_0 = 8$ Hz is a parameters available in the datasheet and $A = 1.5 \times 10^5$ was obtained with the best fit, j is the immaginary unit and f is the frequency. We can see from the plot that our data is consistent with the theory and the datasheet.

For the last two circuit we plotted $H = \frac{v_o}{v_{in}}$, the theoretical curve is the following:

$$H(f) = \frac{\frac{A_{ol}}{1+A_{ol}\beta}}{1 + j \frac{f}{(1+A_{ol}\beta)f_0}}$$

Experiment 5

Introducing the comparator

We first built a relaxation oscillator with different periods, then we tested the LM311 comparator and used it for designing a switch that goes on and off depending on the environment light.

5.1 Materials

- Comparator $\mu A741$
- Operational amplifier LM311
- Phototransistor OP550A
- Resistors, trimmer, LED, capacitors
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Oscilloscope RIGOL MS02102A

5.2 Experimental setup

 


Figure 5.1: Relaxation oscillator

EXPERIMENT 5. INTRODUCING THE COMPARATOR

At first we used the $\mu A741$ (powered with ± 15 V) as a comparator in order to build a relaxation oscillator producing a square wave from a capacitor charge and discharge: we chose $R_1 = R_2 = 10k\Omega$ and a 0.1 nF capacitor. The circuit has been tested with 5 different values of R in order to have different periods. A measure has been taken also setting the oscilloscope in single mode and then switching on the power supply.

We than tested the LM311 both as non-inverting and inverting comparator using $R_L = 1k\Omega$.

Regarding the Schmitt's trigger, we added to the previous circuit the resistences $R_1 = 10k\Omega$ and $R_2 = 100\Omega$ and analyzed the behaviour at the point when $v_{in} \approx v_{ref}$.

 


Figure 5.2: Comparator test with and without Schmitt's trigger

At last, we built the twilight switch in circuit 5.3. We used a phototransistor, which give us a costant current based on the light, a op-amp stage for converting the current in voltage, due to the fact that che current of the phototransistor is very small we had to adjust the offset of the op-amp for avoiding sistematic errors. In the last stage we used a comparator for switch a led on and off comparing a voltage reference v_{ref} with the op-amp stage output.

 


Figure 5.3: Twilight switch

5.3 Data Analysis

 


Figure 5.4: op-amp output v_o and capacitor voltage v_c with $R = 10\text{k}\Omega$

The period of the oscillator is related to the resistor R as follows:

$$T = 2RC \log \left(1 + \frac{2R_1}{R_2} \right)$$

where C is the capacitor and $R_1 = R_2 = 10\text{k}\Omega$. Using the value measured with the multimeter with plot a theoretical curve in function of R . We can see that the data are on that line. We've not done a regression because we did not have the error on the periods.

 


Figure 5.5: Data (green dots) and theoretical curve (blue line)

In the following figures we can see the difference in the comparator output with and without the Schmitt's trigger. If there's not the Schmitt's trigger, the noise can cause a non desired on-off

EXPERIMENT 5. INTRODUCING THE COMPARATOR

switching. The Schmitt's trigger raise and lower the threshold of the switching for avoiding this kind of problems.

 


Figure 5.6: Without Schmitt's trigger


 


Figure 5.7: With Schmitt's trigger

The Twilight switch worked, it was turning on when we were covering the phototransistor and we were able to choose the threshold for the switching by adjusting the voltage reference v_{ref} . Below a photo of this circuit.

 

Experiment 6

Resistance thermometer

We can manage to measure a temperature analysing the voltage drop between the ends of a resistor in which flows a known current, having the resistance depending on temperature by a fixed formula. We build this electronic thermometer, testing during the process the new components.

6.1 Materials

- Operational amplifiers OP07
- Instrumentation amplifier (INA) AD622
- Precision +5V Voltage Reference REF02
- thermistor PT100
- Resistors, trimmers
- Power supply RIGOL DP831A
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068

MANCANO VALORI ED ERRORI

6.2 Experimental setup