

Experiment 1

ADC tracking

In this experience we built an 8-bit ADC tracking with the output switching from 0 and 5 volt (TTL logic).

1.1 Materials

- Resistors, capacitors
- Power supply RIGOL DP831A
- 5V power supply NI myDAQ
- Waveform generator RIGOL DG1032
- Multimeter RIGOL DM3068
- Digital counter (from previous experiment)
- DAC08
- 8-bit LED viewer
- Comparator LM311

The resistors used were all with an uncertainty of 5%

1.2 Experimental setup

First of all we tested our DAC08 powering it with $\pm 15V$ and setting the input current in the $+V_{Ref}$ pin to 2mA: this was achieved by using a 4.4V voltage from the RIGOL power supply and a resistor of $2.2k\Omega$. In order to clear as much as possible the bias current effects, we used another identical resistor between the $-V_{Ref}$ pin and ground and also added a 10nF capacitor between the COMP pin and -15V to optimize the behavior of the component.

Since we used TTL logic and only one output, we put to ground both the V_{LC} and the $\overline{I_{Out}}$ pins.

At this point we had an output current, but we desired an output voltage: for that reason we added a $2081.7 \pm 0.4\Omega$ resistor between the I_{Out} pin and ground.

We then tested the component with various different inputs and measured its resolution.

Once done these measurements we connected the counter circuit from last experiment as the DAC08 input, verifying the output to be a sawtooth signal.

Finally we connected this output to a comparator together with the input voltage to be converted, obtained from the -15V power supply voltage with a $5.6k\Omega$ resistor and a $5k\Omega$ trimmer (therefore freely variable), and used this new output as the $\overline{Up}/Down$ counter input, removing the D-FlipFlop being now useless its signal slowing function.

We chose different signals at different frequencies and visualized them with the 8-bit LED viewer. We

Comparing the results in these last 2 tables, we can see that the measurements are sufficiently compatible with the expected values (with the only exception of the zero-scale that theoretically should be zero with no uncertainty at all).

We can as well measure the resolution of our converter: it is actually the least difference that we can distinguish between two different outputs. Making an average, we come to the result of $1\text{LSB} = 16.72 \pm 0.12 \text{ mV}$

Then, connected the DAC08 to the counter and verified the signal tracking and "capture" feature of our system, we observed the response to a 0.3V continue input, using a 30Hz clock frequency and setting the oscilloscope time scale to 20ms/div. We obtained the graphic shown in figure 11.2



Figure 1.2: signal tracking and "capture" feature of our circuit with a constant input